

ISTANBUL TECHNICAL UNIVERSITY
COMPUTER ENGINEERING DEPARTMENT

BLG 242E
DIGITAL CIRCUITS LABORATORY
EXPERIMENT REPORT

EXPERIMENT NO : 6
EXPERIMENT DATE : 28.05.2020
LAB SESSION : FRIDAY - 13.30
GROUP NO : G11

GROUP MEMBERS:

150180064 : MELİS GÜNŞEBER
150170043 : EBRAR ÖMER
150140902 : PERİT JAN AYDEMİR

SPRING 2020

Contents

FRONT COVER

CONTENTS

1	INTRODUCTION	1
1.1	AND Gate	1
1.2	OR Gate	1
1.3	NOT Gate	1
2	MATERIALS AND METHODS	2
2.1	Experiment I – SR Latch	2
2.2	Experiment II – SR Latch with and Enable Input	3
2.3	Experiment III – DD Flip Flop from D Latches	4
2.3.1	D Latch	4
2.3.2	Negative Triggered D Flip Flop	4
2.4	Part 4	5
3	RESULTS	6
3.1	SR Latch Simulation	6
3.2	SR Latch with Enable Simulation	8
3.3	Negative Triggered D Flip-Flop Simulation	9
3.4	Part 4 Simulation	10
3.4.1	1/2 Frequency Simulation	12
3.4.2	1/4 Frequency Simulation	13
3.4.3	1/8 Frequency Simulation	13
3.4.4	1/3 Pulse-Gap Simulation	14
3.4.5	1/7 Pulse-Gap Simulation	14
4	DISCUSSION	14
5	CONCLUSION	15
6	REFERENCES	15

1 INTRODUCTION

The main goal of this experiment is to implement latches and flip-flops using the Verilog software. This is an introduction experiment for us to use and learn the usage and functions of the Verilog. We have imported our basic modules from the previous experiment as can be seen below.

1.1 AND Gate

```
1 module and_gate(  
2     input A,  
3     input B,  
4     output C  
5 );  
6     assign C = A & B;  
7 endmodule
```

1.2 OR Gate

```
1 module or_gate(  
2     input A,  
3     input B,  
4     output C  
5 );  
6     assign C=A|B;  
7 endmodule
```

1.3 NOT Gate

```
1 module not_gate(  
2     input A,  
3     output B  
4 );  
5     assign B=~A;  
6 endmodule
```

2 MATERIALS AND METHODS

2.1 Experiment I – SR Latch

In the first part, we implemented a SR latch using only NOR gates. The S and R are our inputs. Q and Q n are our outputs. There is not any enable input in this latch design.

Verilog Code

```
1 module sr_latch(  
2     input S,  
3     input R,  
4     output Q,  
5     output Qn  
6 );  
7 wire q1,qn1;  
8 or_gate or1(S,Q,qn1);  
9 not_gate not1(qn1,Qn);  
10 or_gate or2(R, Qn, q1);  
11 not_gate not2(q1,Q);  
12 endmodule
```

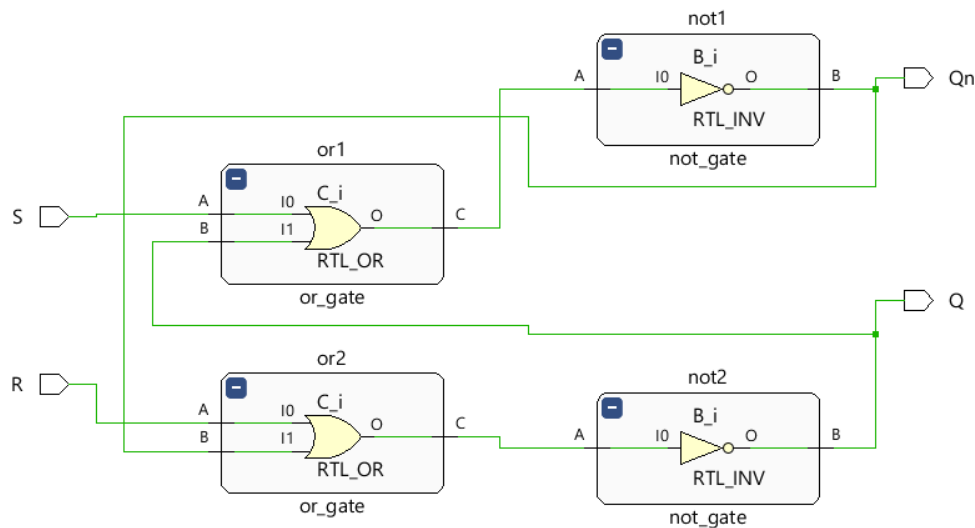


Figure 1: SR Latch

We have defined the inputs S, R and the output as Q and Qn. And after that, we have send S and Q to an OR gate, Q and Qn to NOT gates and R and Qn to an Or gate.

2.2 Experiment II – SR Latch with and Enable Input

In this part, similarly like the previous part we implemented a SR latch but with an enable input with only using NAND gates. The S and R are our inputs. Q and Qn are our outputs.

Verilog Code

```
1 module sr_latch_enabled(  
2     input A,  
3     input B,  
4     input C,  
5     output Q,  
6     output Qn  
7 );  
8  
9     wire S, R;  
10    wire s,r,q,qn;  
11  
12    and_gate s1(A,C,s); not_gate s2(s,S);  
13    and_gate r1(B,C,r); not_gate r2(r,R);  
14    and_gate out1(S,Qn,q); not_gate out2(q,Q);  
15    and_gate comp1(R,Q,qn); not_gate comp2(qn,Qn)
```

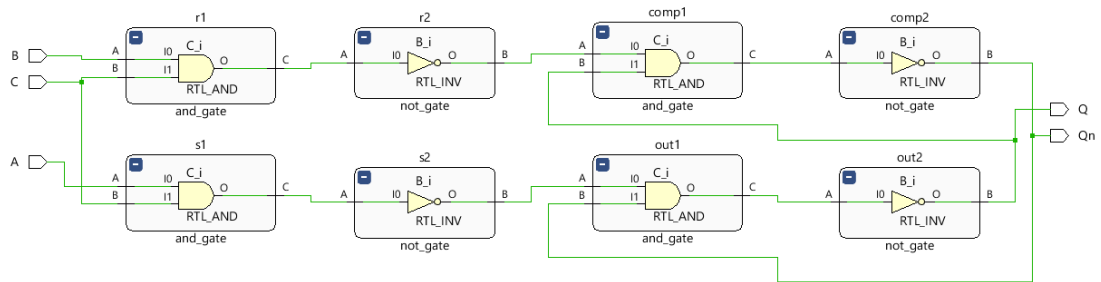


Figure 2: SR Latch with Enable Input

We have defined the inputs A, B and C. C is our enable input and we implemented outputs as Q and Qn. This time we used S and R as wires. Wires only carry A and B's values if the C is enabled.

2.3 Experiment III – DD Flip Flop from D Latches

In this part, we implemented a negative edge triggered D Flip Flop from D latches. The D is our input. Q and Qn are our outputs. We have implemented D latches with only NAND and NOT gates with enable inputs.

2.3.1 D Latch

```
1 module D_latch(  
2     input D,  
3     input En,  
4     output Q,  
5     output Qn  
6 );  
7 wire R;  
8 not_gate n1(D,R);  
9 sr_latch_enabled s(D,R,En,Q,Qn);  
10  
11 endmodule
```

 


Figure 3: D Latch

As seen above we have used SR latch within the D latch.

2.3.2 Negative Triggered D Flip Flop

```
1 module Triggered_D(input D,input CLK, output Q, output Qn);  
2     wire Clk_new, Qm, Qmn;  
3     not_gate clk_n(CLK,Clk_new);  
4     D_latch d1(D,CLK,Qm, QMn);  
5     D_latch d2(Qm,Clk_new,Q,Qn);  
6 endmodule
```

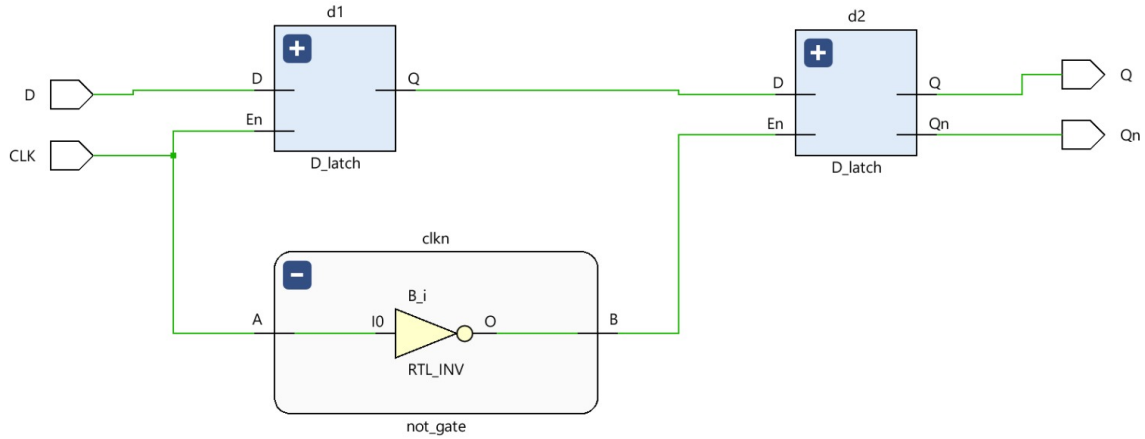


Figure 4: Negative Triggered D Flip-Flop

2.4 Part 4

In this part, we implemented a pulse generator with circular shift register module. The implementation is built to support all the variable pulse frequencies and durations. The D is our input. Q and Qn are our outputs. We have implemented D latches with only NAND and NOT gates with enable inputs. We have a 8-bit input, a 1-bit load input, a CLK input and a 1-bit output. First, we load our 8 bit input and we record the most significant bit, shift all the rest bits to 1-bit left and then add the most significant bit to the end.

```

1 module loadshift (Inp,C,L, S0);
2 input [7:0] Inp;
3 input C,L;
4 output S0;
5 reg [7:0] tmp;
6 reg hold;
7 always @(posedge C)
8     if (L) begin
9         tmp=Inp;
10        // hold=tmp[0];
11    end
12    else begin
13        hold=tmp[7];
14        tmp = tmp << 1;
15        tmp[0]=hold;
16    end
17    assign S0=hold;
18 endmodule

```

3 RESULTS

3.1 SR Latch Simulation

```

1 module sr_test();
2     reg S;
3     reg R;
4     wire Q;
5     wire Qn;
6
7     sr_latch uut(S, R,Q,Qn);
8     initial begin
9         S =1;    R=0;    #200;
10        S =0;    R=0;    #200;
11        S =0;    R=1;    #200;
12        S =0;    R=0;    #200;
13        S =1;    R=1;    #200; //forbidden
14    end
15 endmodule

```


Truth Table of SR Latch

S	R	Q	Qn
0	0	1	0
0	1	0	1
1	0	1	0
1	1	0	0

 


Figure 5: SR Latch Simulation

3.2 SR Latch with Enable Simulation

```
1 module sr_enable_test();
2     reg S;
3     reg R;
4     reg C;
5     wire Q;
6     wire Qn;
7
8     sr_latch_enabled uut(S, R,C,Q,Qn);
9     initial begin
10         S =0;    R=0;    C=0;    #150; //memory
11         S =1;    R=0;    C=1;    #150;
12         S =0;    R=1;    C=1;    #150;
13         S =0;    R=0;    C=1;    #150;
14         S =0;    R=0;    C=0;    #150; //memory
15         S =1;    R=1;    C=1;    #150; //forbidden
16     end
17 endmodule
```

Truth Table of SR Latch with Enable

S	R	En	Q	Qn
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	0	1
1	0	0	0	0
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

 


Figure 6: SR Latch with Enable Simulation

3.3 Negative Triggered D Flip-Flop Simulation

```

1  module D_latch(
2      input D,
3      input En,
4      output Q,
5      output Qn
6  );
7      wire R;
8      not_gate n1(D,R);
9      sr_latch_enabled s(D,R,En,Q,Qn);
10
11  endmodule
12
13  module Triggered_D(input D,input CLK, output Q, output Qn);
14      wire Clk_new, Qm, Qmn;
15      not_gate clk_n(CLK,Clk_new);
16      D_latch d1(D,Clk_new,Qm, QMn);
17      D_latch d2(Qm,CLK,Q,Qn);
18  endmodule

```

 


Figure 7: Negative Triggered D Flip-Flop

3.4 Part 4 Simulation

For each signal, observe both input and output. When Load=0 (that is, shift=1), circular shift operation is done, when Load=1, input value is loaded. in the shift operation or the value been loaded in the load operation. This circuit is positive edge triggered. Hint: You can analyze the internal structure of 74XX165 IC for pulse-generator.

```

1 module ls_test();
2     reg [7:0] signal;
3     reg clock;
4     reg load;
5     wire outp;
6     loadshift deneme(signal, clock, load, outp);
7     initial begin
8         signal=8'b10101010 ;
9         clock=1; load=1; #50;
10        clock =0;#50;
11        clock=1; load=0;#50;
12        clock=0; #50; clock=1; #50;
13        clock=0; #50; clock=1; #50;
14        clock=0; #50; clock=1; #50;
15        clock=0; #50; clock=1; #50;
16        clock=0; #50; clock=1; #50;
17        clock=0; #50; clock=1; #50;
18        clock=0; #50; clock=1; #50;
19        clock=0; #150;
20    end
21    initial begin
22        signal=8'b11001100 ;
23        clock=1; load=1; #50;

```

```

24         clock =0;#50;
25         clock=1; load=0;#50;
26         clock=0; #50; clock=1; #50;
27         clock=0; #50; clock=1; #50;
28         clock=0; #50; clock=1; #50;
29         clock=0; #50; clock=1; #50;
30         clock=0; #50; clock=1; #50;
31         clock=0; #50; clock=1; #50;
32         clock=0; #50; clock=1; #50;
33         clock=0; #150;
34     end
35     initial begin
36         signal=8'b11110000 ;
37         clock=1; load=1; #50;
38         clock =0;#50;
39         clock=1; load=0;#50;
40         clock=0; #50; clock=1; #50;
41         clock=0; #50; clock=1; #50;
42         clock=0; #50; clock=1; #50;
43         clock=0; #50; clock=1; #50;
44         clock=0; #50; clock=1; #50;
45         clock=0; #50; clock=1; #50;
46         clock=0; #50; clock=1; #50;
47         clock=0; #150;
48     end
49     initial begin
50         signal=8'b10001000 ;
51         clock=1; load=1; #50;
52         clock =0;#50;
53         clock=1; load=0;#50;
54         clock=0; #50; clock=1; #50;
55         clock=0; #50; clock=1; #50;
56         clock=0; #50; clock=1; #50;
57         clock=0; #50; clock=1; #50;
58         clock=0; #50; clock=1; #50;
59         clock=0; #50; clock=1; #50;
60         clock=0; #50; clock=1; #50;
61         clock=0; #150;
62     end
63     initial begin

```

```

64     signal=8'b10000000 ;
65     clock=1; load=1; #50;
66     clock =0;#50;
67     clock=1; load=0;#50;
68     clock=0; #50; clock=1; #50;
69     clock=0; #50; clock=1; #50;
70     clock=0; #50; clock=1; #50;
71     clock=0; #50; clock=1; #50;
72     clock=0; #50; clock=1; #50;
73     clock=0; #50; clock=1; #50;
74     clock=0; #50; clock=1; #50;
75     clock=0; #150;
76     end
77
78 endmodule

```

3.4.1 1/2 Frequency Simulation

 


Figure 8: 1/2 Frequency Simulation

3.4.2 1/4 Frequency Simulation

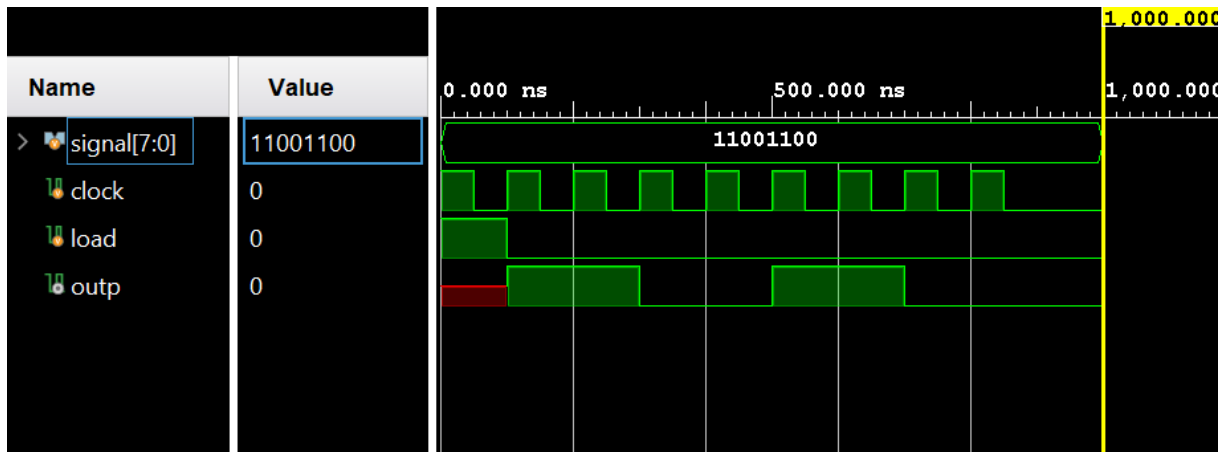


Figure 9: 1/4 Frequency Simulation

3.4.3 1/8 Frequency Simulation

 


Figure 10: 1/8 Frequency Simulation

3.4.4 1/3 Pulse-Gap Simulation



Figure 11: 1/3 Pulse-Gap Simulation

3.4.5 1/7 Pulse-Gap Simulation

 


Figure 12: 1/7 Pulse-Gap Simulation

4 DISCUSSION

First of all, we have imported our simple logical units (AND Gate, OR Gate, NOT Gate) from our previous experiment after that we have designed simple SR memory unit using only NOR gates. After that, we have added an enable button to our SR latch. And then, we have implemented a slightly complex D latch module using SR latch and a NOT Gate. After that, we have designed a Negative Triggered D Flip-Flop using two D latches. Now we have all the requirements to build a 8 bit circular shifter module with pulse generator. The last complex module consists all our previously implemented modules.

5 CONCLUSION

We imported our simple modules from previous experiment and by using them we have created larger modules. We implemented inner circuitry of memory units and observed their behaviour. Building larger modules we have observed that, many complex design is made by simple elements. We used enable input and CLK signal and interpreted them and in the simulations we observed that how crucial they are.

6 REFERENCES